 


# COOK-BOOK OF NARROWBAND LNA



## **Report Presented by:**

Bishal Paudel

M.TECH in RF and Microwave

Department of Electronics & Electrical Communication Engineering

IIT Kharagpur

## 1. CS Stage with Inductive Degeneration:

In the pursuit to find best design topology for LNA, we have concluded Inductive degeneration LNA to be our strategy in week 5 report.

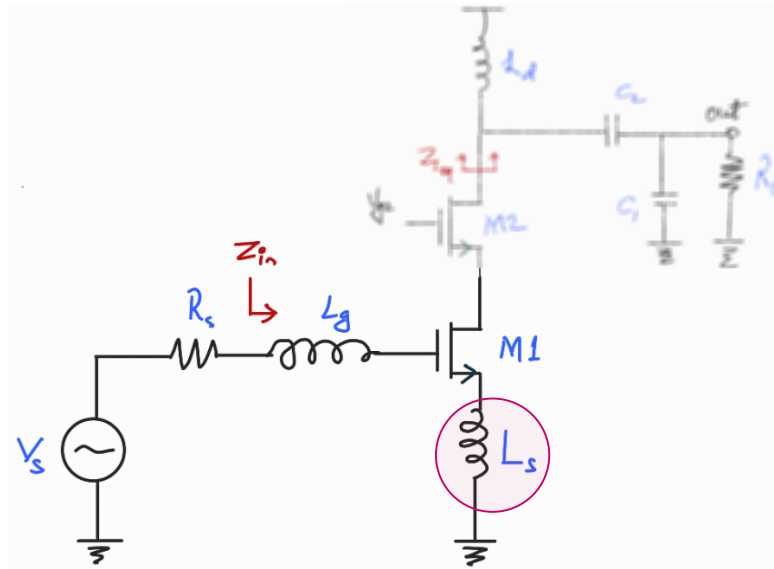


Figure 1: CS Amplifier with Inductive Degeneration as LNA

Till now we have just made a **Low noise** Trans-conductor i.e., we have converted the voltage to the current but the gain of the device shown in Figure 1, doesn't come up to the mark of our LNA requirement.

## 2. Complete LNA: Cascode Topology:

For contentment of gain requirement, we can have multiple transistors in Cascode Topology.

### Why Cascode?

- Reduces Miller effect on  $M_1$ . (Miller effect in MOSFET accounts for an increase in input Capacitance i.e.,  $C_{gs}$  caused by the gain of the amplifier)
- Provides good reverse isolation. ( $S_{12}$  is low)

- Amplifier is unilateral (signal only flows from input to output)
- Allows the input match to be independent of the output match.

Our strategy is to, have a cascode device on the drain of  $M_1$ , put a load at the drain of  $M_2$  which will be matched to have a maximum power transferred.

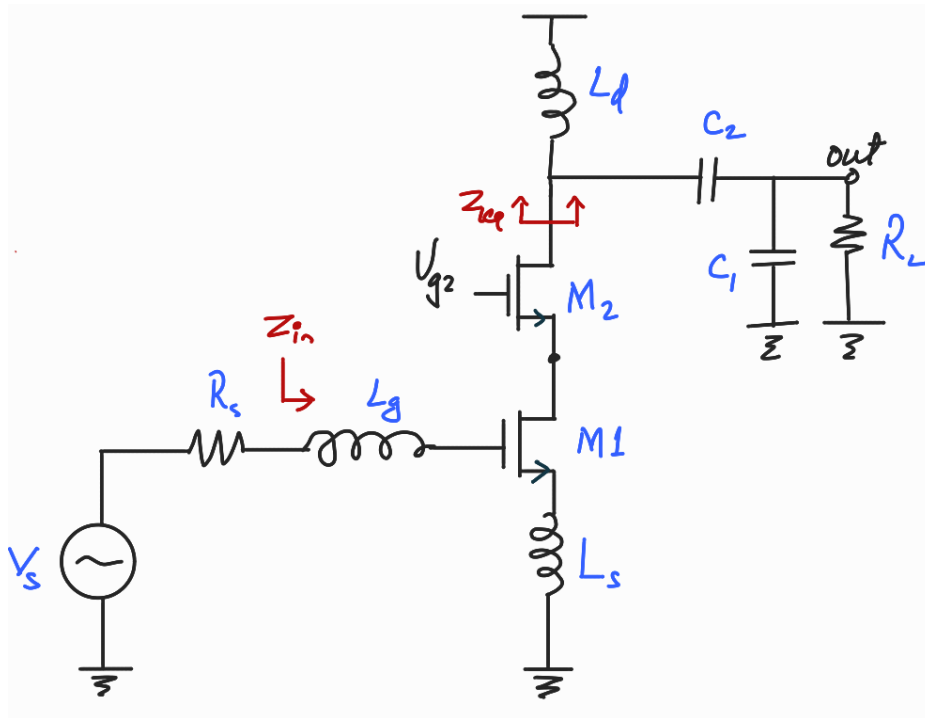



Figure 2: A Complete LNA: Cascode Topology

### 3. Gain Analysis of Cascode LNA:

Let's divide gain analysis in stages, for easier computation of total gain.

$$|A_v| = \left| \underbrace{\left( \frac{V_{gs1}}{V_s} \right)}_{(a)} \underbrace{\left( \frac{V_{d1}}{V_{gs1}} \right)}_{(b)} \underbrace{\left( \frac{V_{d2}}{V_{d1}} \right)}_{(c)} \underbrace{\left( \frac{V_{out}}{V_{d2}} \right)}_{(d)} \right|$$

(a)  $\left| \left( \frac{V_{gs1}}{V_s} \right) \right| \Rightarrow$  series resonant circuit at input.

 


$$\begin{aligned} \left| \left( \frac{V_{gs1}}{V_s} \right) \right| &= \frac{1/\omega_0 C_{gs}}{R_s + \omega_T L_s + \cancel{j\omega(L_g + L_s)} + \cancel{1/j\omega C_{gs}}} \\ &= \frac{1/\omega_0 C_{gs}}{R_s + \omega_T L_s} \\ &= \frac{1}{\omega_0 C_{gs}(R_s + \omega_T L_s)} = Q_{in}^* \end{aligned}$$

Under Resonance


\* $Q_{in}$  of input resonance circuit tends to give us voltage amplification. And it sounds like a **free gain** but it comes with a **cost of Bandwidth**. But if narrowband is needed we get nice gain characteristics for sure.

(b)  $\left| \left( \frac{V_{d1}}{V_{gs1}} \right) \right| \cong \frac{1}{\frac{g_{m2} + j\omega_0(C_{gs2} + C_p)}{-\frac{1}{j\omega_0}}} = \frac{g_{m1}}{g_{m2}} |\delta(\omega)|$

 

where;

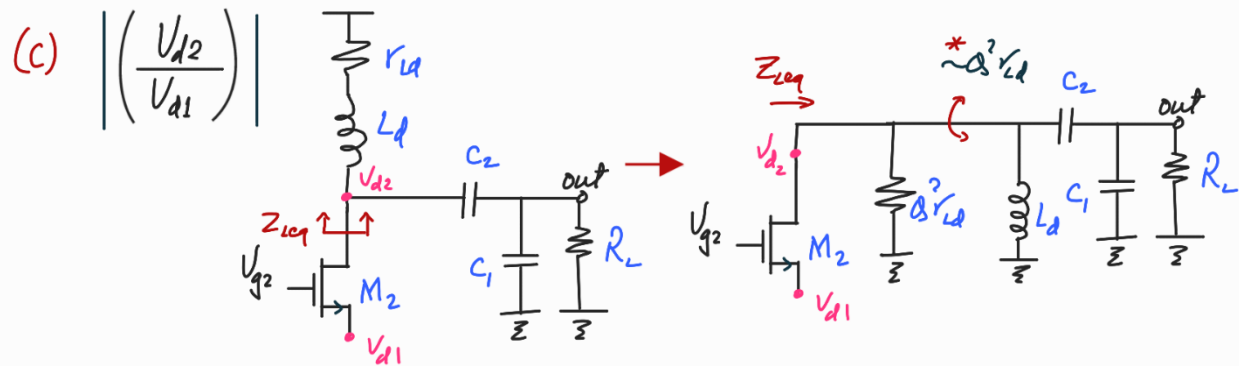- $\delta(\omega) = \frac{g_{m2}}{g_{m2} + j\omega_0(C_{gs2} + C_p)}$   
↑  
**LPF Response**
- $C_p = \text{Parasitic Capacitance}$   
 (Such as Interconnect Capacitance)




$$\therefore \left| \left( \frac{V_{d2}}{V_{d1}} \right) \right| = \frac{\frac{1}{2} Q^2 r_{Ld}}{1/g_{m2}} = \frac{1}{2} g_{m2} Q^2 r_{Ld}$$

Where,  $r_{Ld}$  is a parasitic resistance of a practical inductor  $L_d$ .

\*After series parallel conversion (ref week8) of  $r_{Ld}$  to  $Q^2 r_{Ld}$  comparatively it is very small so it become dominant. So, we will match the Load resistance  $R_L$  with  $Q^2 r_{Ld}$  which makes  $Z_{Leq} = 0.5 * Q^2 r_{Ld}$

(d)

$$\left| \left( \frac{V_{out}}{V_{d2}} \right) \right| = \frac{\frac{R_L}{1 + j\omega C_1 R_L}}{\frac{R_L}{1 + j\omega C_1 R_L} + \frac{1}{j\omega C_2}} = \frac{j\omega C_2 R_L}{1 + j\omega (C_1 + C_2) R_L} = \frac{1}{n(\omega)}$$

 

where,

$$n(\omega) = \text{Complex turns ratio} \\ = \frac{1 + j\omega (C_1 + C_2) R_L}{j\omega C_2 R_L}$$

This  $C_1, C_2$  combination is known as a **capacitive transformer**.

Wont the  $C_1$  of capacitive transformer drain all the RF signal to ground?

= No, because  $n(\omega) \rightarrow 1 + \frac{C_1}{C_2}$  when,  $\omega \rightarrow \infty$  So the capacitive transformer is actually Independent of frequency.

## Final Gain Expression

Substituting the previous four expressions.

$$|A_v| = (Q_{in}) \left( \frac{g_{m1}}{g_{m2}} |S(\omega)| \right) \left( \frac{1}{2} \cancel{g_{m2}} Q_{Ld}^2 r_{Ld} \right) \left( \frac{1}{|n(\omega)|} \right)$$

$$= \frac{1}{2} Q_{in} g_{m1} Q_{Ld}^2 r_{Ld} \left| \frac{S(\omega)}{n(\omega)} \right|$$

Substituting  $Q_{in}$  &  $Q^2 r = Q \omega_0 L_d$  &  $\omega_T = \frac{g_m}{C_{gs}}$

$$|A_v| = \frac{1}{2} \left( \frac{\omega_T Q_{Ld} L_d}{R_s + \omega_T L_s} \right) \left| \frac{S(\omega)}{n(\omega)} \right|$$


### Ways to maximize Gain:

- Maximize  $\omega_T$ 
  - We can make  $\omega_T$  larger by making device larger which improves  $g_{m1}$  but  $Q_{in}$  is going to degrade because  $C_{gs}$  will also increase.
  - So, we will keep the size same but increase the current with **biasing** then  $Q_{in}$  remains the same but  $g_m$  goes up so does  $\omega_T$
- Maximize inductor quality factor ( $Q_{Ld}$ )
- Maximize  $L_d$
- Maximize  $\delta(\omega)$ , meaning resonate out  $C_p$
- Trade-off  $S_{11}$  for increased  $S_{21}$  i.e., reduce value of  $L_s$ 
  - The purpose of source degenerated inductor  $L_s$  is to match with  $50\Omega$  which will give me great  $S_{11}$  but as a last resort we can decrease  $L_s$  as a trade-off between  $S_{21}$  and  $S_{11}$

## 4. Cookbook of Unilateral (Cascode) Source-Degenerated LNA:

This procedure is for Narrow-Band LNA's.

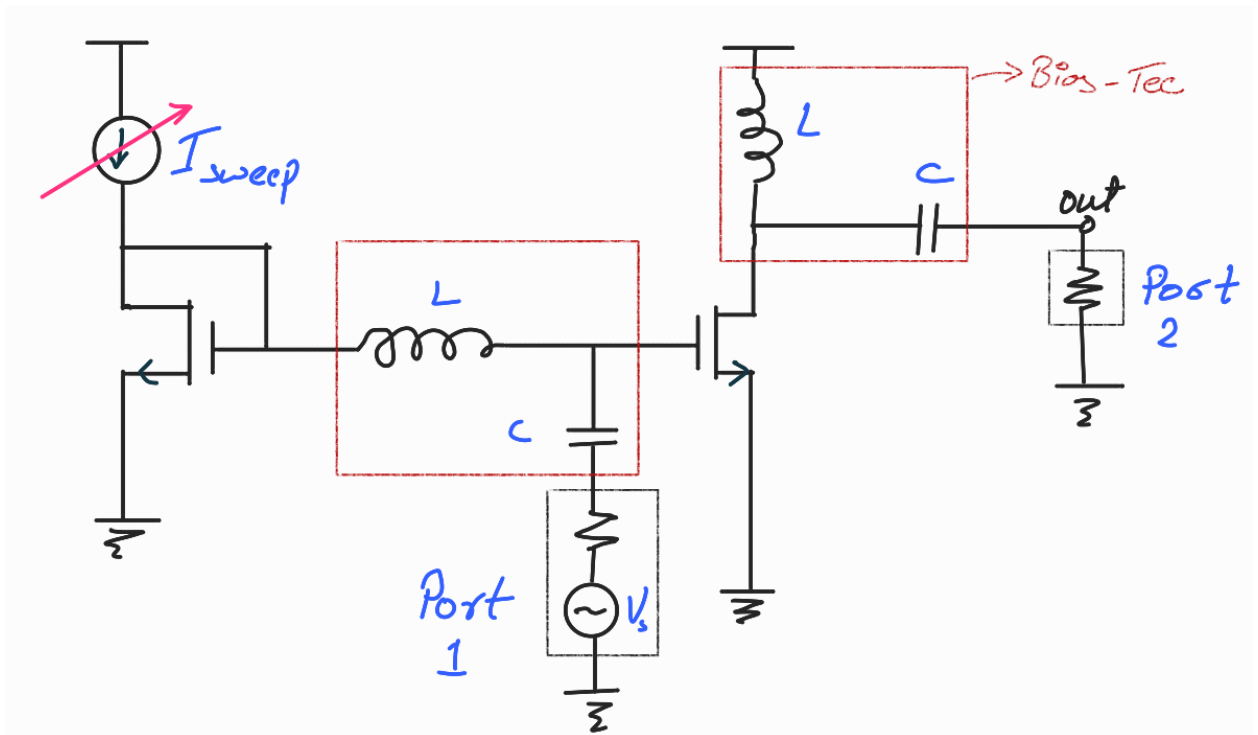1. Create current mirror circuit with bias-T's and sweep bias to find optimum current for  $NF_{min}$




Where, L and C will be kept as 1H and 1F respectively.


- Bias-Tee is there to block RF with inductor and block DC with capacitor.
- Now simulate **single finger** FET and sweep bias current to find optimum current density range for minimum noise i.e., plot  $NF_{min}$  vs  $I_{ref}$
 
### 2. Add cascode( $M_2$ )

- Add cascode device( $M_2$ ) nominally of same size as  $M_1$ . You can alter the size for better performance later. We could have gone for cascode in 1<sup>st</sup> step only but now we can know how much noise is cascode presenting and repeat the same



 3. Update bias network (use resistive choke rather than  $L_{\text{big}}$  in I/P only)






- **Finalize** bias network design, nominally a cascode current mirror coupled to  $M_1$  through a moderate-value resistor ( $\sim 5 \text{ k}\Omega$ ).

Wait won't this resistor ( $R_{\text{choke}}$ ) create a noise?


= Yes, It will

 

And is very less as  $V_A = \frac{V_n^2 \times 50}{5K + 50}$


But if you decrease the size of  $R_{\text{choke}}$  the noise factor will increase.
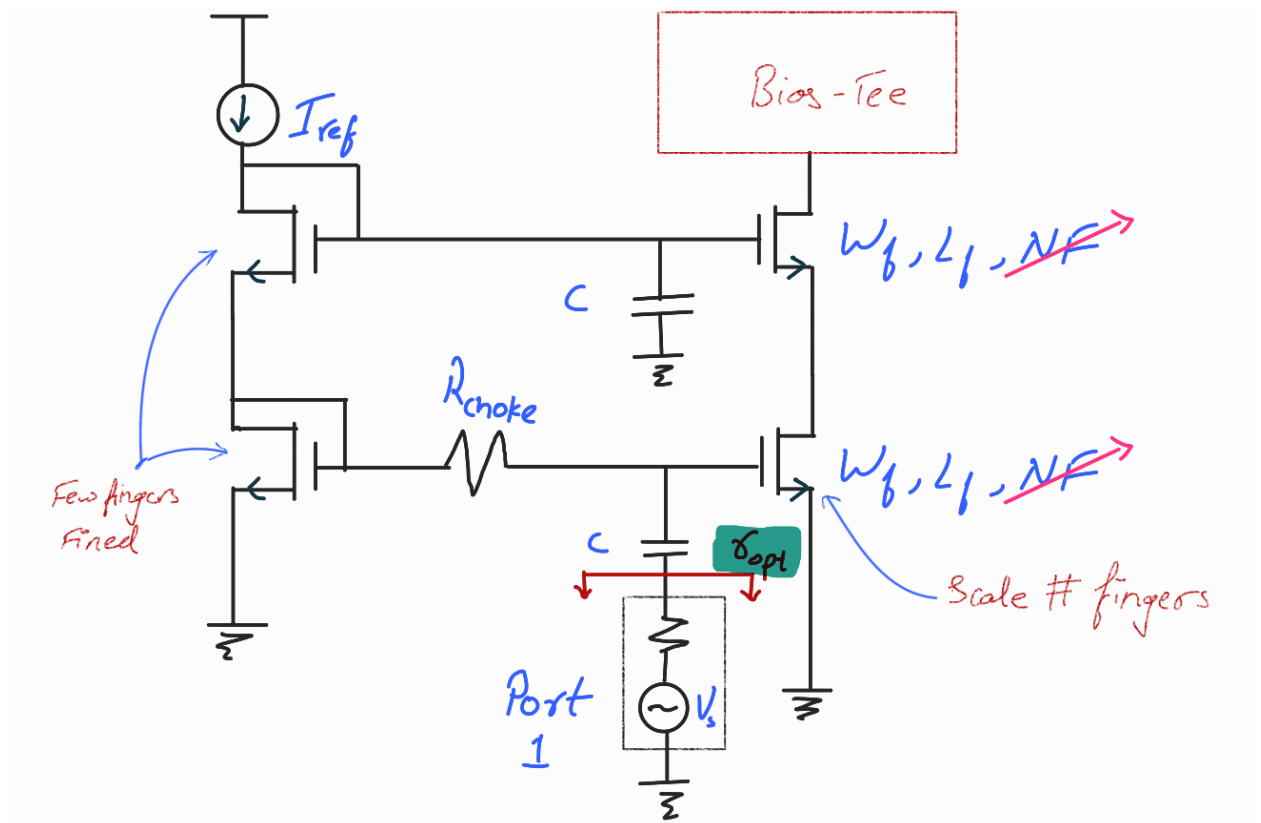
#### 4. Scale size to get $R_{\text{opt}}$ (Noise Match)





- Scale the number of fingers until  $R_{\text{opt}}$  (optimum noise resistance) is close to  $50 \Omega$ . The cascoded transistor  $M_2$  is kept as same size as  $M_1$
- Plot fingers vs  $R_{\text{opt}}$  plot to find the optimum value for fingers
 
## 5. Add $L_s$ to generate real $Z_{in}$ (Power match)



- Add degeneration inductor ( $L_s$ ) to provide real input impedance close to  $50\ \Omega$ . Degeneration can be either on-chip spiral or bond wire.
- This step gives me optimum power match i.e.,  $\text{Re}[Z_{in}] = 50\ \Omega$

## 6. Add $L_g$ to complete input match

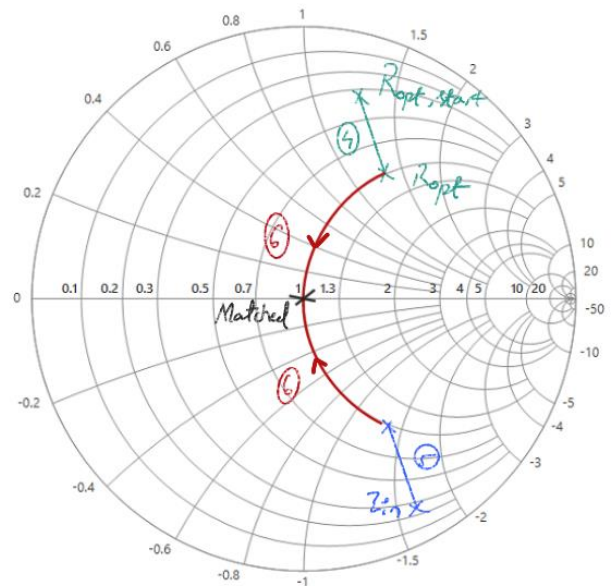 

- So, **step 4** will bring  $R_{opt}$  to constant  $50\ \Omega$  circle and **step 5** will bring  $\text{Re}[Z_{in}]$  to constant  $50\ \Omega$  circle.
- And finally **step 6** will bring both  $R_{opt}$  and  $\text{Re}[Z_{in}]$  to **matched condition**.

7. Design  $L_d$  spiral inductor. Add parasitic resistor
8. Simulate output impedance  $Z_{out}$  and design output matching network ( $C_1$  and  $C_2$ ).
9. Simulate  $IIP_3$  and  $P_{1dB}$  and compare with requirement, increase bias current as required.
10. Simulate all specifications over process, voltage, temperature (PVT)
  - Note that the PVT simulations can/should be embedded with each step to ensure all along that the design is sufficient. This can be achieved with parametric simulation.